

Title of the Exercise: Scott Connection of Transformer



Date: 10/11/2020

Aim: To obtain balanced two-phase supply from three-phase supply by Scott arrangement of two single phase transformers

Tool used : MATLAB and SIMULINK

Electrical Circuit:

Scott Connection or T-T Connection

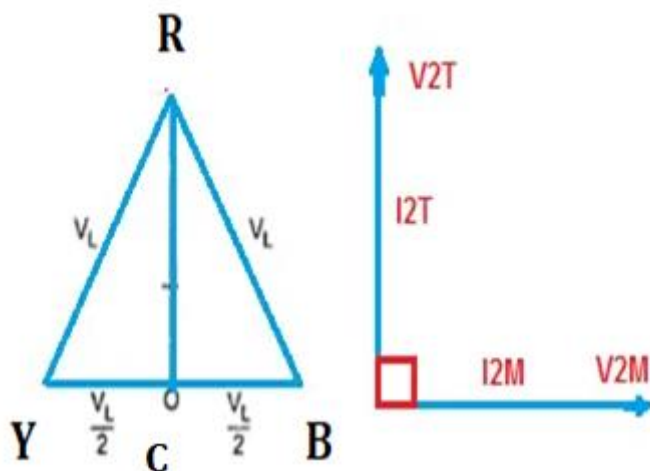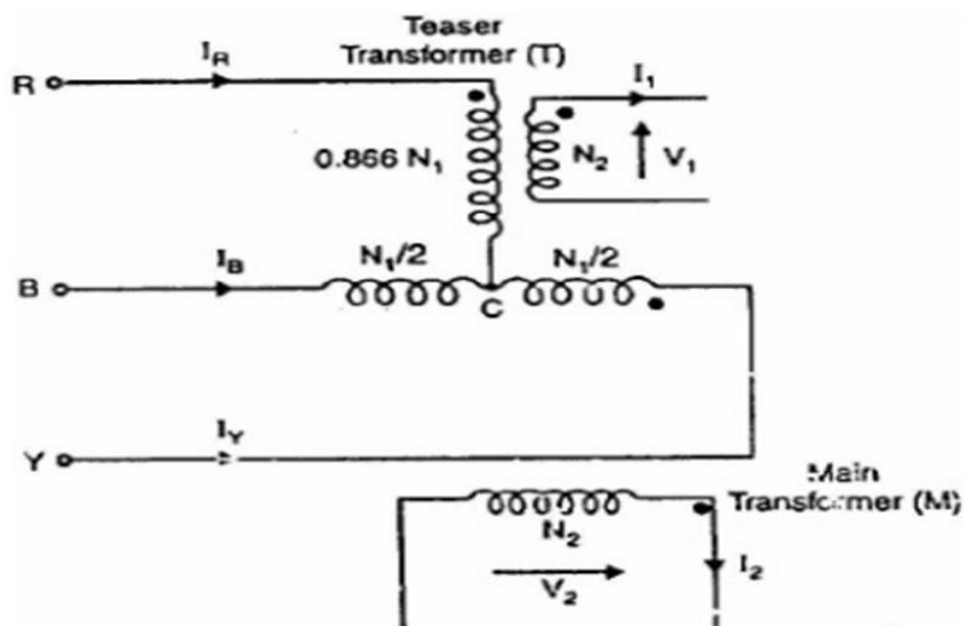

Parameters used for the study:

Transformer rating = 25KVA

$V_{RB} = V_{BY} = V_{YR} = 400V$ (primary voltage in Rms)

Frequency $f = 50$ Hz

Transformer ratio = 2

$R_1 = 0.7488$ ohm (Primary winding resistance)

$X_{11} = 1.00224$ ohm (Primary winding reactance)

$R_2 = 0.007488$ ohm (Secondary winding resistance)

$X_{12} = 0.0100224$ ohm (Secondary winding reactance)

$X_M = 5,008$ ohm (Magnetizing reactance)

$R_c = 33,391$ ohm (Resistance for core losses)

Theoretical Analysis:

$$V_{2T} = V_{RC} \frac{N_2}{0.866 N_1}$$

$$V_{RC} = 0.866 V_L$$

$$V_{2T} = V_L \frac{N_2}{N_1}$$

$$V_{2M} = V_{BY} \frac{N_2}{N_1}$$

$$V_{BY} = V_L$$

$$V_{2M} = V_L \frac{N_2}{N_1}$$

$$I_{BY} * N_1 = I_{2M} * N_2$$

$$I_{BY} = I_{2M} \frac{N_2}{N_1}$$

$$I_R * 0.866 * N_1 = I_{2T} * N_2$$

$$I_R = 1.15 * I_{2T} \frac{N_2}{N_1}$$

Calculations (predetermination):

$$\frac{N_2}{N_1} = 2; I_R = 0.06963A$$

$$V_L = V_{BY} = 400V$$

$$V_{RC} = 0.866 * 400 = 364.4V$$

$$V_{2T} = 400 * (2) = 800V$$


$$V_{2M} = 400 * 2 = 800V$$

$$I_{2T} = 0.06963 * 0.866 * 0.5 = 0.3015A$$

Procedure:


- Step1-Initialize the input parameters and write coding for the as per requirement of plots in m file and save it.
- Step 2-open new Simulink and make mathematical modelling as per circuit diagram and save it
- Step 3-Run the Simulink file.
- Step 4- Get the plots from the corresponding scopes.

Simulink file:

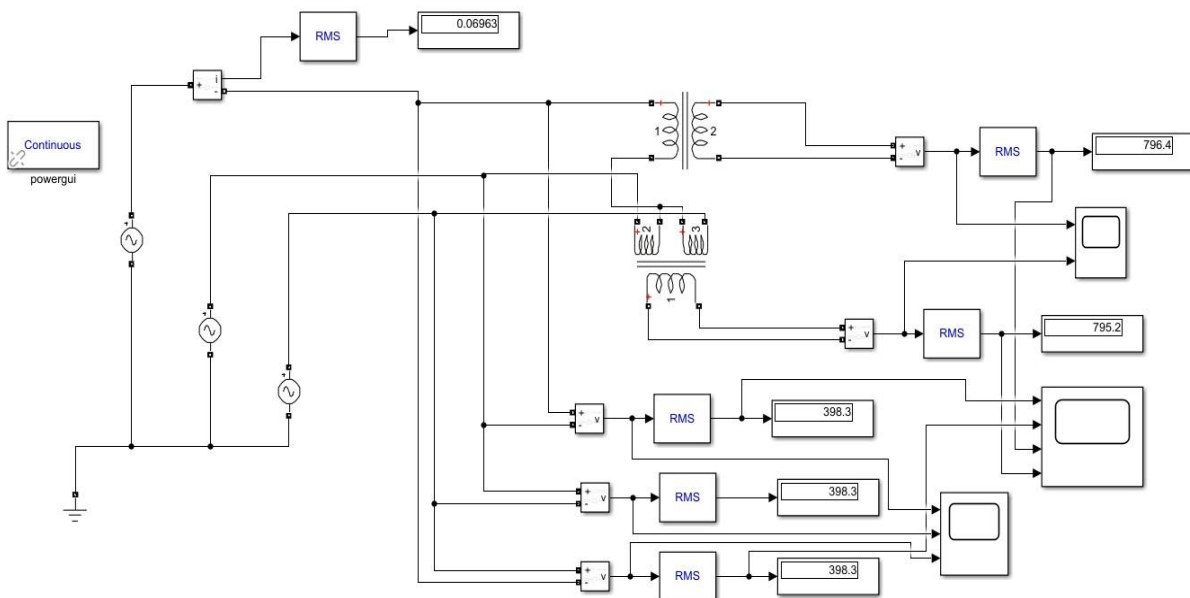


Result:


Three phase input voltage

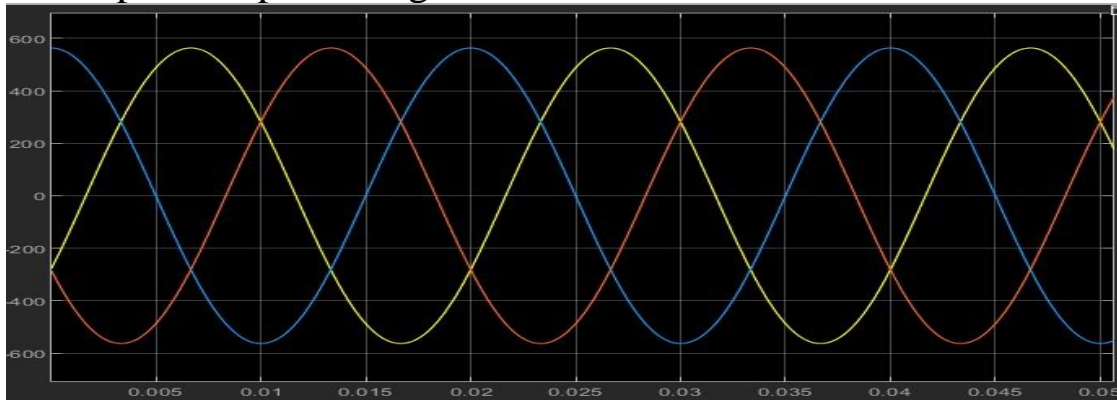

Two phase output voltage

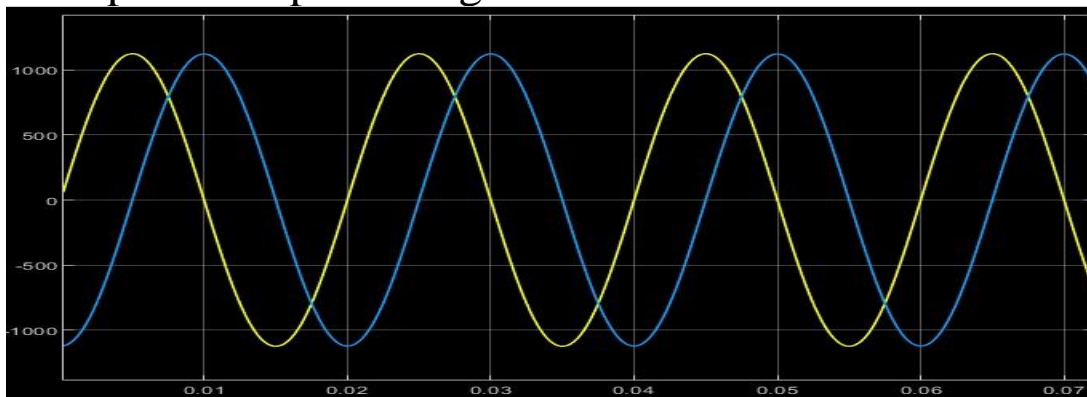

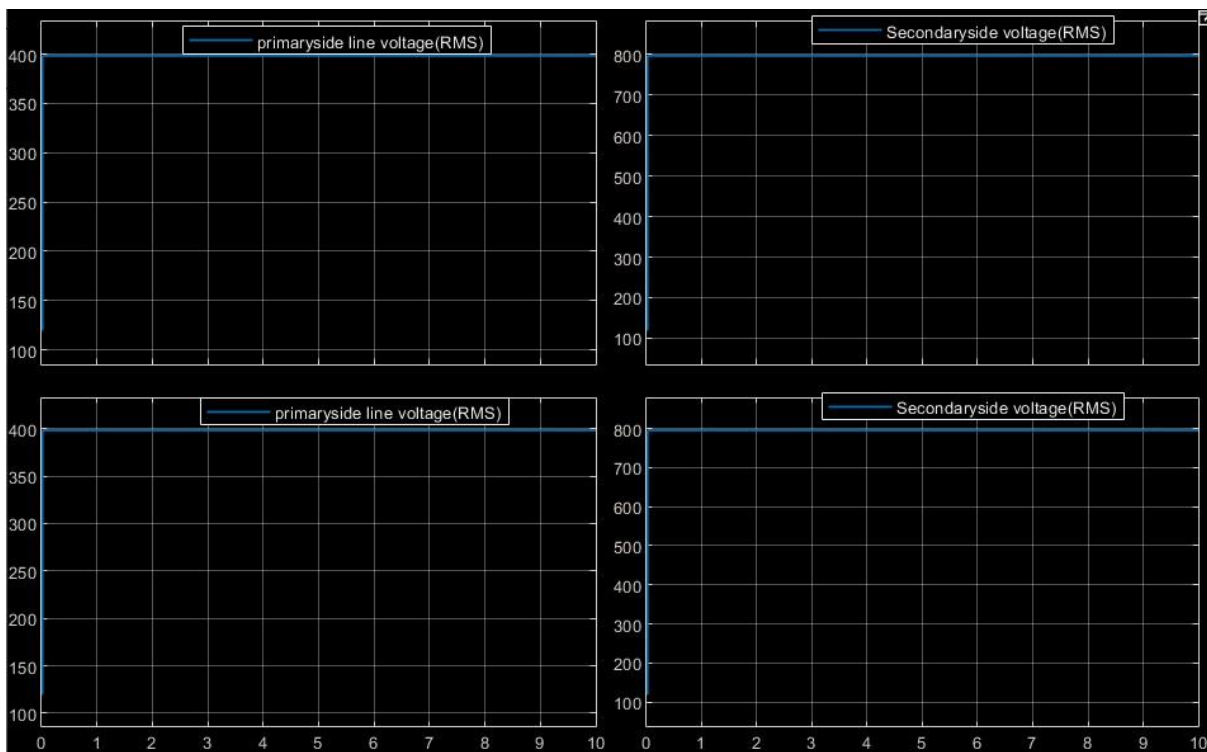Primary side and secondary side line voltage(rms)



Observations:

Parameters	Theoretical values(V)	Simulation values(V)
V_L	400	398.3
V_{2T}	800	796.4
V_{2R}	800	795.9

Conclusion:

Hence, two-phase supply is obtained from three phase supply using Scott arrangement of two single phase transformers.

Inference:

Therefore, the theoretical values of line voltage nearly matches with simulation ones.

References:

- <https://in.mathworks.com/>
- Analysis and design of control systems using MATLAB – By Rao V.Dukkipati